



assume I as shown.

loop \mathcal{R} from a:

$$-IR_1 - \mathcal{E} - IR_2 = 0$$

$$\text{So: } I = \frac{-\mathcal{E}}{R_1 + R_2} = \underline{\underline{-0.5\text{A}}}$$

Negative \Rightarrow CCW

Potential across each resistor:

$$\Delta V_1 = IR_1 = \underline{\underline{20\text{V}}}$$

$$\Delta V_2 = IR_2 = \underline{\underline{30\text{V}}}$$