



Assume I as shown.

Loop eqn \mathcal{R} from a: $-IR - \mathcal{E}_2 + \mathcal{E}_1 = 0$

$$\therefore I = \frac{\mathcal{E}_1 + \mathcal{E}_2}{R} = \underline{\underline{-0.5 A}}$$

Negative sign \Rightarrow current is opposite what was assumed

\therefore current right \rightarrow left through the resistor

or, CCW