



Need to find  $I_1$ ,  $I_2$  &  $I_3$

Junction at b:  $\sum I_{in} = \sum I_{out}$   
 $I_1 = I_2 + I_3$  (1)

Loop Equ'n  $\curvearrowright$  from b (outer)

$$-I_3 R_4 - I_1 R_3 + \mathcal{E} - I_1 R_1 = 0 \quad (2)$$

Loop Equ'n  $\curvearrowright$  from b (left)

$$-I_3 R_4 + I_2 R_2 = 0 \quad (3)$$

subst. (1)  $\rightarrow$  (2):

$$-I_3 R_4 - (I_2 + I_3) R_3 + \mathcal{E} - (I_2 + I_3) R_1 = 0$$

$$-I_3 R_4 - I_2 R_3 - I_3 R_3 - I_2 R_1 - I_3 R_1 + \mathcal{E} = 0$$

or

$$-I_2 (R_3 + R_1) - I_3 (R_4 + R_3 + R_1) + \mathcal{E} = 0$$

$$-6 I_2 - 26 I_3 + 100 = 0 \quad (4)$$

Now: equ'n (3) in:

$$-20I_3 + 5I_2 = 0 \quad (5)$$

and (4)  $26I_3 + 6I_2 = 100 \quad (6)$

$$(5) \rightarrow I_2 = \frac{20}{5} I_3 = 4I_3$$

$\rightarrow (6)$

$$26I_3 + 6(4I_3) = 100$$

$$50I_3 = 100$$

$$\therefore \underline{I_3 = 2A}$$

Now:

$$\underline{I_2 = 4I_3 = 8A}$$

and

$$\underline{I_1 = I_2 + I_3 = 10A}$$

a)  $I_1 = 10A$  through  $2\Omega$  resistor

b)  $P_1 = I_1^2 R_1 = 200W$

c)  $P_2 = I_2^2 R_2 = 60W$

$P_3 = I_3^2 R_3 = 60W$