



For \$R_4\$ to dissipate no power, must have \$I_2 = 0\$.

junction at a: $I_1 = I_2 + I_3 \Rightarrow I_1 = I_3$

Left loop \$\mathcal{R}\$ from a: $-I_2 R_2 + \mathcal{E}_1 - I_1 R_1 = 0$

So: $I_1 = \frac{\mathcal{E}_1}{R_1} = 0.5 A = I_3$

Now, right loop \$\mathcal{R}\$ from a: (assume \$E\$ has + on top and - on bottom)

$-I_3 R_3 - \mathcal{E} + I_2 R_2 = 0$

$\mathcal{E} = -I_3 R_3 = -150 V$

So, $\mathcal{E} = 150 V$, but it is oriented with - on top and + on bottom.