



Find P_1 and P_2 , the power dissipated in the resistors.

Why can't we use:

$$P_1 = \frac{\Delta V^2}{R_1} = \frac{\mathcal{E}^2}{R_1} \quad \& \quad P_2 = \frac{\Delta V^2}{R_2} = \frac{\mathcal{E}^2}{R_2} \quad ?$$

The ΔV 's in these equations must be the potentials across the resistors which aren't \mathcal{E} .

Need to find I , which is the same for each R :

Loop \square from a: $+ \mathcal{E} - IR_1 - IR_2 = 0$

$$\text{So, } I = \frac{\mathcal{E}}{R_1 + R_2} = 0.4 A$$

$$\therefore P_1 = I^2 R_1 = \underline{1.92 W}$$

$$P_2 = I^2 R_2 = \underline{2.88 W}$$