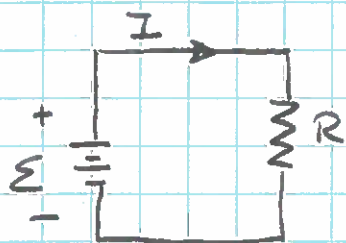


Single Bulb




Loop \square : $-IR + \epsilon = 0 \Rightarrow I = \frac{\epsilon}{R}$

Power of single bulb alone:

$$P_1 = I^2 R = \frac{\epsilon^2}{R^2} R = \frac{\epsilon^2}{R}$$

Series:

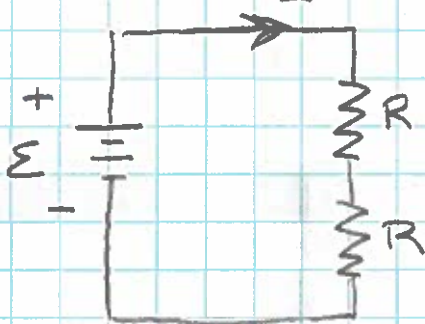

Loop \square : $-IR - IR + \epsilon = 0$


$$\Rightarrow I = \frac{\epsilon}{2R}$$

Power of one bulb in series:

$$P_{\text{series}} = I^2 R = \frac{\epsilon^2}{4R^2} R = \frac{1}{4} \frac{\epsilon^2}{R} = \frac{P_1}{4}$$

So, bulb is 1/4 as bright.

Parallel:

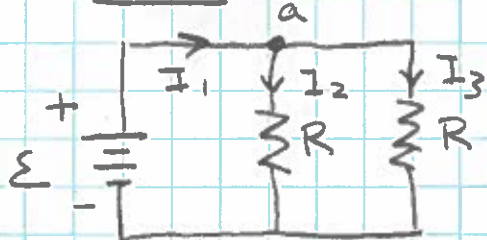

left loop \square from a: $-I_2 R + \epsilon = 0$

$$\Rightarrow I_2 = \frac{\epsilon}{R}$$

right loop \square a: $-I_3 R + I_2 R = 0$

$$\Rightarrow I_3 = I_2 = \epsilon/R$$

So, power on either bulb is:

$$P_{\text{par}} = I_2^2 R = \frac{\epsilon^2}{R^2} R = \frac{\epsilon^2}{R} = P_1$$

same as for one bulb alone.

But, total current, $I = I_2 + I_3 = 2\epsilon/R$