



at $t = 2\text{ms}$, $\frac{Q}{Q_0} = 0.1$

$$Q(t) = Q_0 e^{-t/\tau}$$

So: $\frac{Q}{Q_0} = 0.1 = e^{-t/\tau}$

$$-\frac{t}{\tau} = \ln(0.1)$$

and

$$\tau = \frac{-t}{\ln(0.1)} = 0.868\text{ms}$$

$$= 8.68 \times 10^{-4}\text{s}$$

So:

$$\tau = RC \Rightarrow R = \frac{\tau}{C} = \underline{\underline{868.6\ \Omega}}$$