

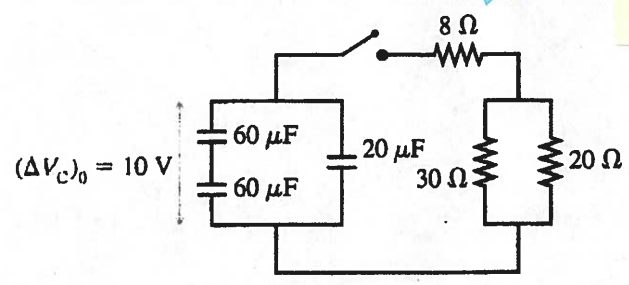
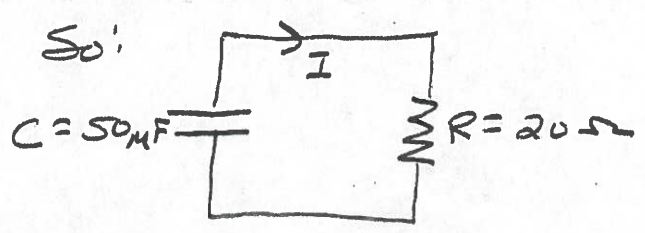


WB 28-13
1

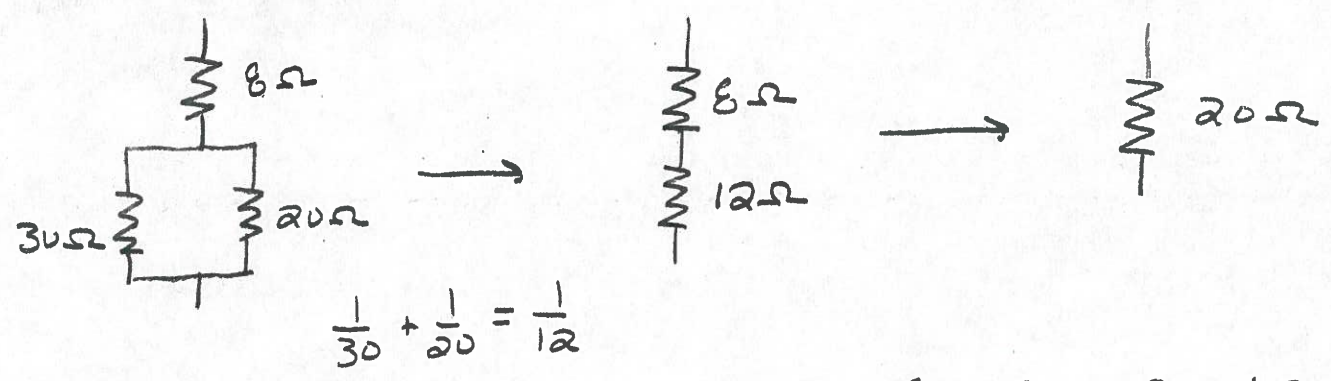

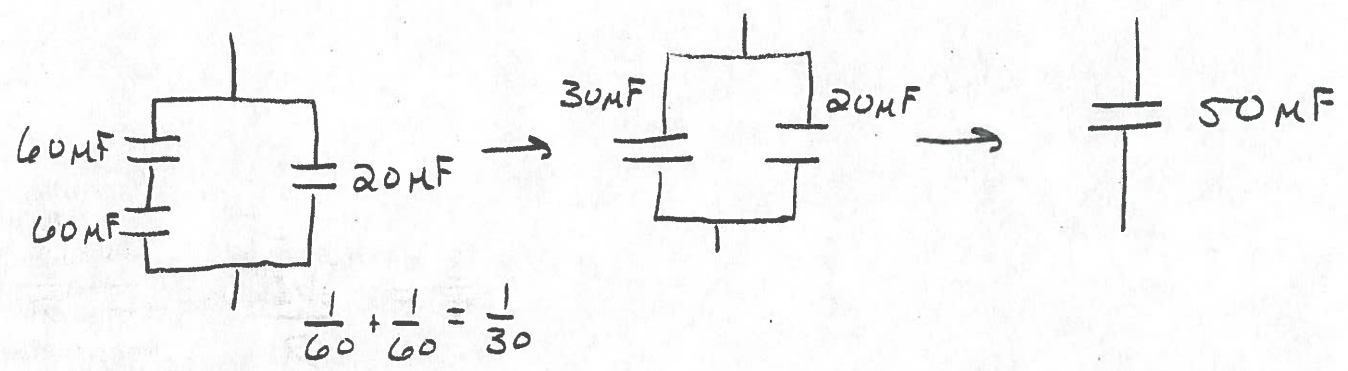To find time constant, combine capacitors and resistors:



$$\tau = RC = 0.001 \text{ s}$$

and

$$I = I_0 e^{-t/\tau}$$

$$\frac{I}{I_0} = \frac{1}{2} = e^{-t/\tau}$$

$$\ln\left(\frac{1}{2}\right) = -\frac{t}{\tau} \Rightarrow t = -\tau \ln\left(\frac{1}{2}\right)$$

$$= 6.93 \times 10^{-4} \text{ s}$$